

- Question 1:** Fig 1 shows a special circuit where the diode D denotes an ideal diode. The initial values of the circuit are zero. Compute the time-domain response of the voltage v_{C1} when a step change of 1 A is applied to its input current. Utilize the basic relation between the capacitor current and voltage for solving the problem. Sketch the waveform of v_{C1} .

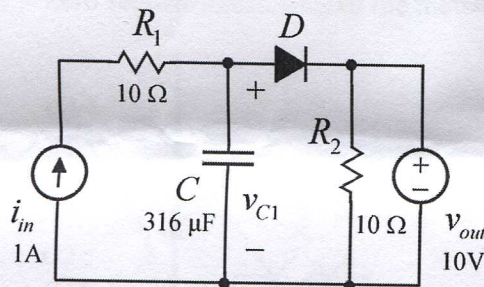


Fig. 1. The circuit of question 1.

- Question 2:** A three-phase load is fed through a three-phase feeder. The source phase voltage of phase a at the feeding end of the feeder is $325\cos(377t+55^\circ)\text{V}$. The feeder is 1.5 km long, having parameters $R = 1.3 \Omega/\text{km}$ and $X = 0.2 \Omega/\text{km}$. The load is a constant impedance load having impedance of $(10+j4)\Omega/\text{phase}$.
- Draw the single-line diagram of the network and calculate the phase currents. Draw the phasor diagram of the current and voltage of phase a.
 - Calculate the three-phase real power, reactive power, apparent power and power factor of the source.
 - Calculate the three-phase real power, reactive power, apparent power and power factor of the load.

- Question 3:** Fig. 2 presents an electric circuit and all the relevant parameter values are given on the figure.

- Determine the nodal admittance matrix of the electric circuit.
- Calculate the voltage at node 2.
- Determine the powers injected by the two voltage sources at nodes 1 and 3.

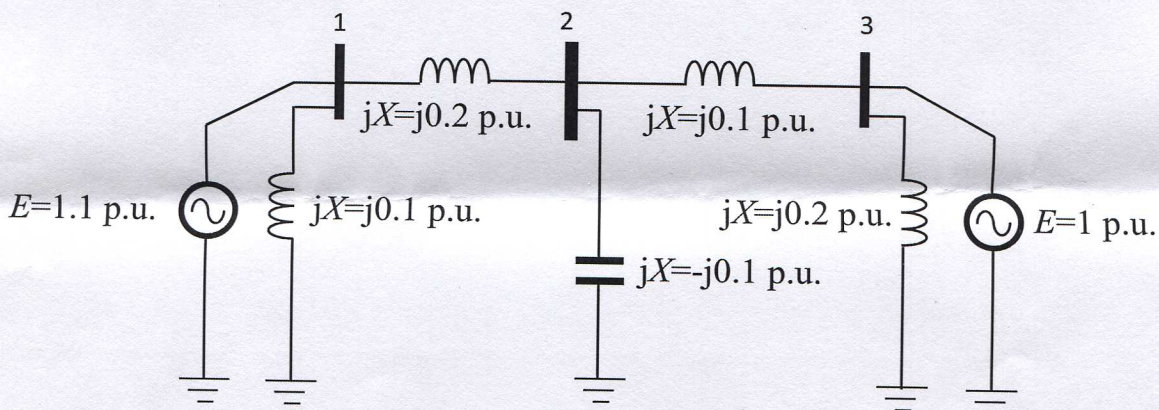


Fig. 2. The electric circuit of question 3.

Question 4: Draw the positive, negative and zero sequence impedance networks for the power system in Fig. 3. Use per unit values.

Generator 1 (G1): 25 MVA, 11 kV, $X'' = 0.15$, $X_2 = 0.1$, $X_0 = 0.03$ pu
Generator 2 (G2): 15 MVA, 11 kV, $X'' = 0.2$, $X_2 = 0.15$, $X_0 = 0.05$ pu
Synchronous motor 1 (M1): 25 MVA, 8 kV, $X'' = 0.2$, $X_2 = 0.2$, $X_0 = 0.1$ pu
Transformer 1 (T1): 50 MVA, 11/220 kV, $X = 8\%$
Transformer 2 (T2): 25 MVA, 220/8 kV, $X = 10\%$
Zero sequence reactance of the transmission line is 230 % of its positive sequence reactance.

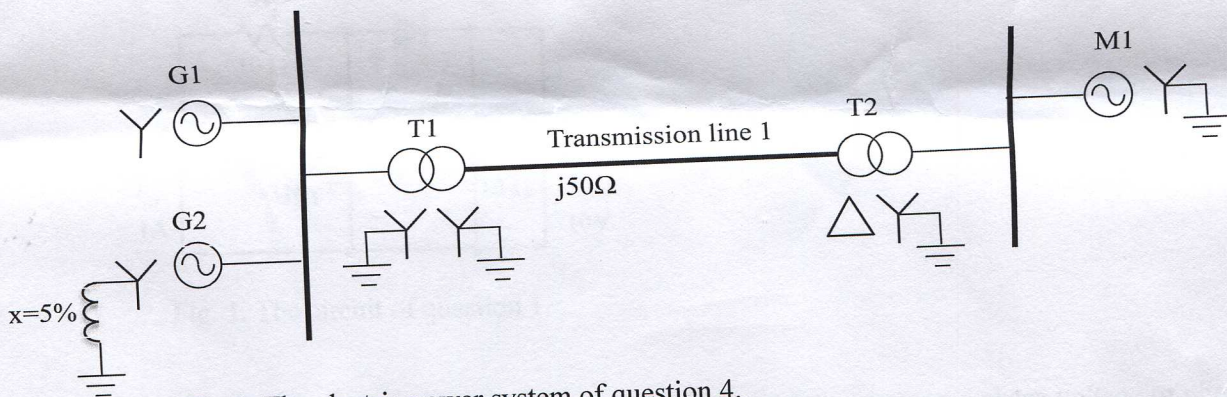


Fig. 3. The electric power system of question 4.

- Question 5:** Plan a high-pass filter using any passive circuit components.
- Draw the circuit diagram and determine the transfer function between output and input voltages u_o/u_{in} .
 - Draw an approximate Bode diagram of your transfer function.
 - Determine such component values that the cutoff frequency of the filter is 350 Hz.