

- Question 1:** A one-phase voltage source is feeding a load through a one-phase feeder. The source voltage is $155.56\cos(377t+10^\circ)\text{V}$. The feeder impedance is $1+j2\ \Omega$ and the load impedance is $10-j4\ \Omega$.
- Draw the circuit diagram of the network and calculate the current. Draw the phasor diagram of the current and voltage. (2p)
 - Determine the real power, reactive power, apparent power and the power factor of the source. Draw the power triangle. (2p)
 - Determine the real power, reactive power, apparent power and the power factor of the load. Draw the power triangle. (2p)

- Question 2:** A three-phase power system consisting of one generator, two transformers, a transmission line and a load is represented in Fig. 1. The parameters of the system are the following:
Generator 1 (G1): 50 MVA, 11 kV, $X_1 = 0.15$, $X_2 = 0.1$, $X_0 = 0.03\text{ pu}$
Transformer 1 (T1): 50 MVA, 11/110 kV, $X = 9\%$
Transformer 2 (T2): 25 MVA, 110/20 kV, $X = 10\%$
Load 1 (L1): $P_{\text{nom}} = 10\text{ MW}$, 20 kV
Load 2 (L2): $Q_{\text{nom}} = 5\text{ MVar}$, 20 kV
- The loads are modeled using a constant impedance load model such that they consume their nominal powers at the nominal voltage. The given power is three-phase power and the voltage 20 kV is the nominal line-to-line voltage. Calculate the impedance values for the loads. (1p)
 - Draw the positive sequence impedance network of the circuit. Use per unit values. (3p)
 - Calculate the current flowing through the transmission line. The internal emf of the synchronous generator G1 can be assumed to be $1.05\angle 0^\circ\text{ pu}$. (2p)

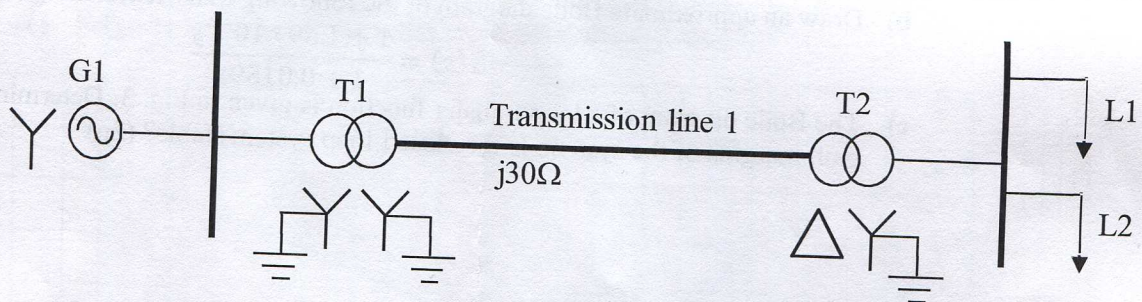


Fig. 1. The power system of question 2.

- Question 3:** Fig. 2 presents an electric circuit and all the relevant parameter values are given on the figure.
- Determine the nodal admittance matrix of the electric circuit. (1p)
 - Calculate the voltages at nodes 3 and 4. (2p)
 - Determine the real and reactive powers injected by the two voltage sources at nodes 1 and 2. (2p)
 - Calculate the powers consumed by the resistive loads R_{30} and R_{40} . (1p)

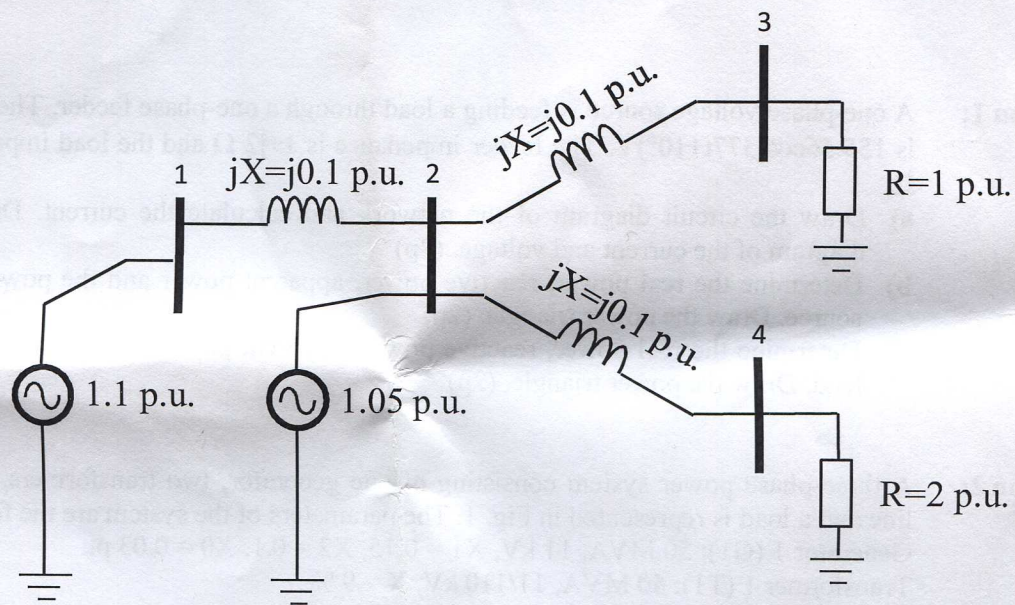


Fig. 2. The electric circuit of question 3.

Question 4:

- a) Find symmetrical components of the following three-phase voltage. Draw the phasor diagrams of the original voltage phasors and the symmetrical components. (2p)

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} 1.05 \angle 10^\circ \\ 0.8 \angle -20^\circ \\ 1.2 \angle 190^\circ \end{bmatrix}$$

- b) Draw an approximate Bode diagram of the following transfer function. (2p)

$$G(s) = \frac{1 + 1.59 \cdot 10^{-4}s}{1 + 0.0159s}$$

- c) The Bode diagram of a loop transfer function is given in Fig. 3. Determine the phase and gain margins of the system. Is the closed-loop system stable? (2p)

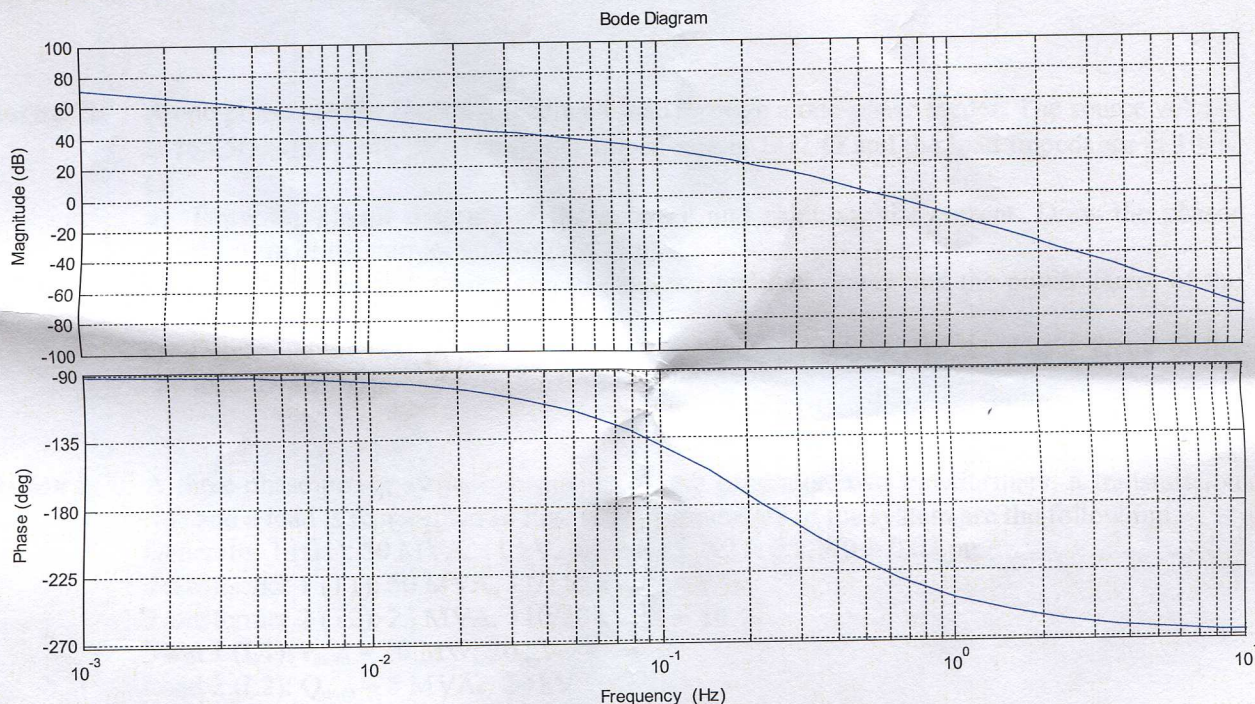


Fig. 3. Bode diagram of question 4c.

Question 5: The frequency response of impedance of a system is shown in Fig. 4. The system is composed of two passive components with their corresponding equivalent series resistances (ESRs).

- What is the circuit? Draw the circuit and write its s-domain impedance equation. (2p)
- Estimate the values of its main passive components. (2p)
- Estimate the value of the ESRs involved in the system. (2p)

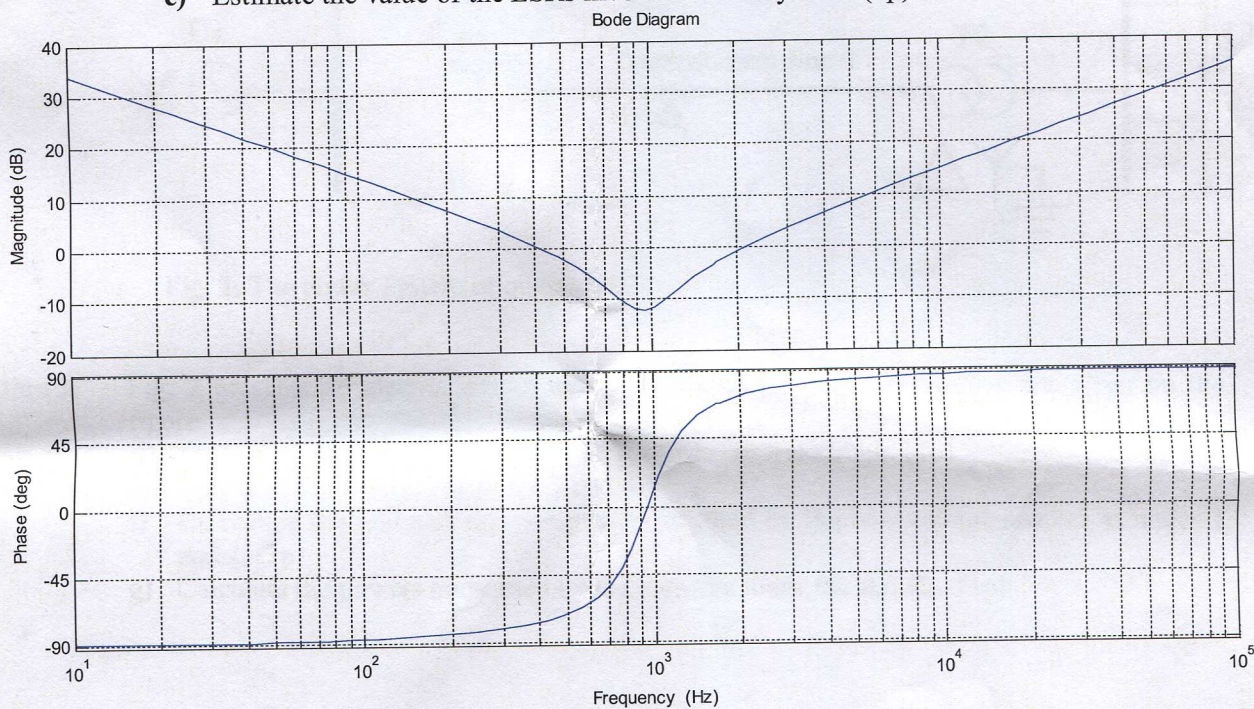


Fig. 4. Impedance plot of question 5.