

Use of own programmable calculator is allowed.

Problem 1 (max 8 points)

Power stage of a voltage-fed inverter with dq-domain output-current control is as shown in Figure 1.

- Develop the inverter average model in dq-domain at open-loop, $\left(\langle i_{in} \rangle = \frac{3}{2} d_d \langle i_{L,d} \rangle + \frac{3}{2} d_q \langle i_{L,q} \rangle \right)$.
- Draw the equivalent linear circuit in dq-domain (DC input port and two AC output ports).
- How do you have to modify the duty ratio d and q-components (by adding x_d and x_q) to make the inverter output currents independent of the grid voltage d and q-components? I.e., how to implement grid voltage feedforward?
- How do you realize decoupling of the current d and q-components? Use the average model to obtain necessary control laws / scaling coefficients.

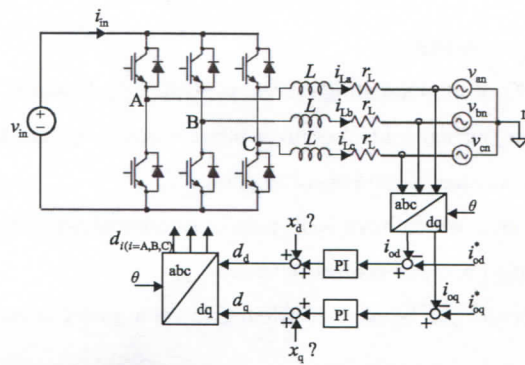


Figure 1: Voltage-fed inverter with output-current control.

Problem 2 (max 4 points)

Instantaneous apparent power can be defined as the product of voltage space-vector and the complex-conjugate of current space-vector in the stationary reference frame as in (1).

- Define real and imaginary power in the synchronous reference frame, i.e., in the dq-domain. The space vector is assumed to rotate at the fundamental grid frequency ω_s .
- Explain (based on the previous result), how the real and imaginary power produced by three-phase inverter can be controlled independently.

$$s = v^{\alpha\beta} \cdot (i^{\alpha\beta})^* \quad (1)$$

Problem 3 (max 6 points)

Control block diagram of a phase-locked-loop is as shown in Figure 2. The feedforward term ω_{ff} is a constant which improves start-up. The Park's transformation can be linearized as $\hat{v}'_q = \hat{v}_q - V_d \hat{\theta}$ where \hat{v}_q denotes the ideal grid voltage q-component.

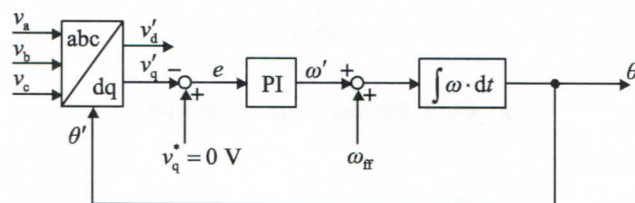


Figure 2: Phase-locked-loop.

- Draw the linearized control block diagram and define control loop gain of the PLL.
- Solve transfer function from the reference input \hat{v}_q^* to the controlled variable \hat{v}_q' in dq-domain.
- The transfer function from reference to the controlled variable can be written as a second-order system as in (2). Find out the damping ratio ζ and natural frequency ω_n in terms of controller parameters. You can assume that the controller transfer function is as given in (3).

$$G = (2\zeta\omega_n s + \omega_n^2) / (s^2 + 2\zeta\omega_n s + \omega_n^2) \quad (2)$$

$$G_c = \frac{(-1) \cdot K(s/\omega_z + 1)}{s} \quad (3)$$

Problem 4 (max 6 points)

Give short answers to following questions.

- What is the main benefit of implementing current control in dq-domain?
- How can one implement current control of three-phase inverter outside dq-domain?
- Why do you need to solve steady-state operating point?
- Can you stabilize converter which has a RHP-pole in its control dynamics? How?
- Give short definition of a cascaded control scheme?
- How should the PLL bandwidth be selected when grid voltages are unbalanced?

Problem 5 (max 6 points)

Figure 3 shows current control loop gain with a simple unity-gain integrator as the controller (4). Comment on the stability and expected performance of the current control. Propose a controller transfer function to increase stability margins and explain how to select controller parameters (poles/zeros/gains). The control loop gain should have a crossover frequency around few kilohertz. You don't need to give specific values for controller parameters. You may sketch bode diagrams to justify the tuning process.

$$L_{out} = G_{cod-o} \cdot \frac{1}{s} \quad (4)$$

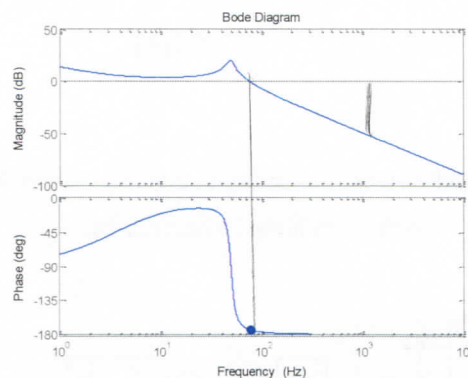


Figure 3: Current control loop gain.